

Matter:

The matter is anything around us that has both mass and volume which occupies space.

For example: A car would be said to be made of matter as it occupies space & has mass. $\rightarrow$ Matter commonly exists in three stages, solid, liquid & gas.

Molecules:

A molecule is an electrical neutral group of two or more atoms held together by covalent chemical bond.

or, A molecule is formed when two or more atoms join together chemically.

A compound is a molecule that contains at least two different elements.

Atom:

The atom is a basic unit of matter that consists of a dense central nucleus surrounded by cloud of negatively charged electron.

The atomic nucleus contains a mixture of positively charged protons & electrically neutral neutrons.

* Electrical charge:

Electrical charge is the physical property of matter that causes it to experience a force which is close to other electrically charged matter.

There are two types of electric charges called +ve and -ve.

+vely charged substances are repelled from other +vely charged substances but -vely charged substances are repelled from -ve charge & attracted to +ve charge.

An object will be -vely charged, if it has an excess of electron & will be otherwise positively charged or, uncharged.

The Unit of electric charge is ^{Coulomb (C)} ~~Columb~~ & it is denoted by Symbol (Q).

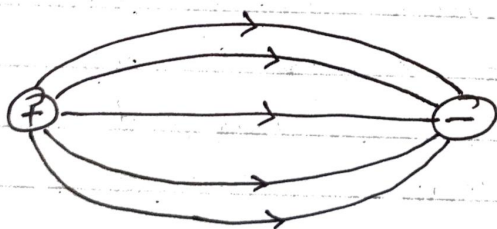


Fig: Electric field of +ve & -ve point charge.

Electric Current:

The drift (flow or, movement) of electrons in any conductor is called electric current.

i.e. the rate of movement of charge (electron)

$$I = \frac{Q}{T} = \frac{dq}{dt} = \frac{\text{Coulomb}}{\text{Second}} = \text{Ampere}$$

Where,

Q or dq be the quantity of charge electricity passed during a given time (t).

Let, in any conductor

n = no. of electrons

available per meter cube

v = Final drift velocity in dt s

ds = distance travelled in dt second by the electron.

i.e. $ds = v \cdot dt$

A = Area of cross-section of the conductor

$$\therefore V = A \times ds = A \times v \cdot dt \quad (\text{Volume})$$

Total number of electrons contained in this volume = $A \cdot v \cdot dt \cdot n$

All these electrons will cross the conductor of cross-section in time dt . dq will be the charge of electrons then total quantity of ~~at~~ charge, which cross the section in the time dt is

$$dq = A \cdot v \cdot dt \cdot n \cdot e \text{ coulomb.}$$

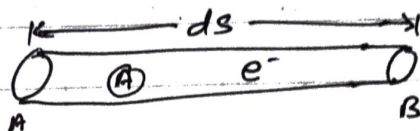


Fig: Conductor

then, by definition; we have

electric current = rate of flow of charge

$$= \frac{A \times v \times dt \times n \times e}{dt}$$

$$= ne v A$$

$$\therefore \boxed{I = ne v A}$$

(I) (N)

The current per unit of area of cross-section of the conductor is called current density and is denoted by J .

$$\text{i.e. } J = \frac{I}{A} = \frac{ne v A}{A}$$


$$= ne v$$

It's unit is (Ampere/m^2) "

Conventional Current versus Electron Flow:

→

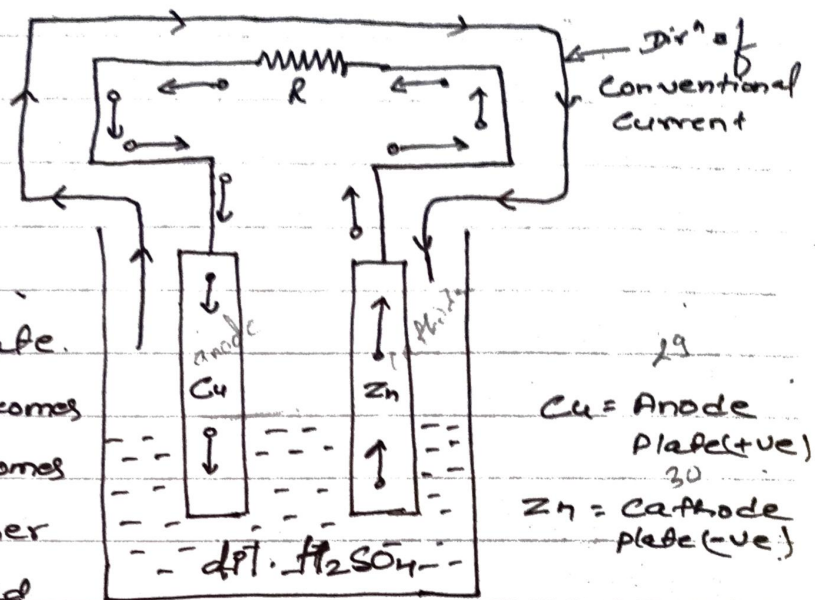Due to dil. H_2SO_4 contained in a vessel; Electron travels from Cu-plate to Zinc plate. So, the Zn-plate becomes -ve and Cu-plate becomes +ve. The large number of electrons collected on Zn plate and being attracted by anode



29
Cu = Anode
Plate (+ve)
30
Zn = Cathode
plate (-ve)

Fig: Voltage Cell
or Voltaic cell

but is prevented from returning to it by the action of dil. H_2SO_4 . When these two electrodes are joined by a wire externally, then electrons rush (try to go fast) to the anode (Cu) These by equalizing the charges.

At the same time chemical action in the vessel transfers electrons from Cu-plate to Zn-plate internally, this process continues as long as there is chemical energy. The flow of electrons through the external wire from Zn-plate to Cu-plate is the electric current (electronic current e^-) (Cathode to anode). A Conventional current flow from Cu to Zn i.e. Anode to Cathode.

* Measurement of Current and Voltage:

- Ammeter is used for the measurement of current and is connected in series.
- Voltmeter is used for measurement of voltage and is connected in parallel.

Potential difference (P.d) or, Voltage (V) & Electromotive force.

- * Potential difference: Potential difference between two points can also be defined as the work done in moving unit positive test charge from one point to another point against electrical force.

[OR]

The difference of electric pressure between any two points of conductor is called P.d.

So, it is that which causes the current to flow in a closed circuit.

It's unit is 'Volt'.

Electromotive force (E.m.f)

It is the force which tends to move the electron in any closed circuit.

[OR]

The force which tends compels the electrons to move in a complete path.

It cannot be measured accurately.

$E.m.f = P.d + \text{Voltage drop inside the Source of Supply.}$

Q) Why E.m.f cannot be measured?

⇒ E.m.f cannot be measured because the instrument which we use to measure, that instrument consume some energy/voltage and doesnot give accurate Voltage.

Conductor, Insulator and Electron flow:

Conductor: The materials that have one or, two valence electron which are free to move in called Conductor.

[OR]

Those substance which offers such a small resistance that rapidly allow electricity to flow through them. Such as Ag, Cu, Al, Au, electrolytes etc.

Insulator/Badconductor: Those materials having ^{no} free electron or more valence electron which are away to be freed.

[OR]

The insulators are those substance which offers

Such a resistance that they allow no flow of electricity through them.

Such as rubber, asbestos, bakelite, all-nonmetals_{etc}

Resistance and its Variation with temperature

Resistance: It is defined as that property of a substance which opposes the flow of electricity (e^-) through it.

It is represented by ' R ' and measured in ohm (Ω) and its ckt. symbol is denoted by



V.I.

* Law of Resistance or,

Factor affecting the value of resistance.

The value of the resistance depends upon the following factors:-

- a) The resistance of the conductor varies directly for its length. i.e. as length increases the resistance also increases.

i.e. $R \propto l$

+ve Temp. Coefficient of resistance : Conductor
-ve " " " : Insulator

b) Resistance of the conductor varies inversely for its cross-section area. i.e. as ^{C.S.} area of the conductor increases then resistance decreases
i.e. $R \propto \frac{1}{A}$

c) Resistance of the conductor depends on the nature of material (ρ) directly.
i.e. $R \propto \rho$

d) Resistance, also depends upon the temperature of the conductor negatively, that factors we can write

$$R \propto \frac{l}{A}$$

$$\text{or, } R = \rho \frac{l}{A} \quad \text{or, } \rho = \frac{RA}{l} \quad \left[\because A = \frac{\pi d^2}{4} \right]$$

Where,

l = length of conductor in m

A = Area of conductor in m^2

ρ = Constant for material. It's value

depends on the nature of material of the conductor in $\Omega\text{-m}$ called its specific resistance or resistivity.




(#) The increase in temperature ~~decrease~~ ^(Pure metal) increases resistance of conductor and decrease in temperature decreases resistance of conductor.
& opposite for insulator.

* Specific resistance or, Resistivity (ρ):

It is defined as the resistance of the pieces of unit length & unit cross-section.

i.e. it is a resistance between the opposite faces of unit ~~of~~ cube of material.

It is measured in $\Omega\text{-m}$.

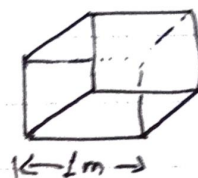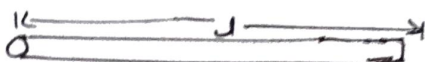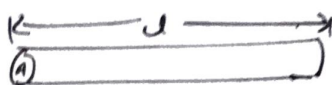

Where,

$$l = 1\text{m}$$

$$A = 1\text{m}^2$$

$$\therefore R = \rho \frac{l}{A} = \rho \frac{1}{1}$$

$$\therefore \boxed{R = \rho}$$

α = the change in resistance per ohm per degree rise of ~~temp~~ at some specified temperature usually 0°C .

* Variation of resistance with temperature: / or Temperature coefficient of resistance (α)

It is defined as the increase in resistance per ohm of original resistance for a rise in temperature of 1°C from 0°C & vice versa.

i.e.

$$\alpha = \frac{\text{Increase in resistance for } 1^\circ\text{C rise in temperature}}{\text{Original resistance at } 0^\circ\text{C}}$$

Consider a piece of copper of resistance $R_0 \Omega$ at 0°C . After heating let R_t be the resistance at $t^\circ\text{C}$ & t be the rise in temperature

In order to estimate the resistance of a conductor at one temperature, having known its resistance at another, the temperature coefficient of material is used.

$\propto \Delta R$

Rise in resistance $\Delta R = R_t - R_0$

- It directly depends upon its original initial resistance,
- directly on the rise of temperature. ($t_2 - t_1 = t$)
- on the nature of the material of conductor.

Hence,

$$R_t - R_0 \propto R_0 \times t$$

$$\text{or } R_t - R_0 = \alpha \cdot R_0 t$$

$$\text{or } R_t = R_0 + \alpha R_0 t$$

$$\text{or } R_t = R_0 (1 + \alpha t) \quad \text{--- (1)}$$
$$= R_0 (1 + \alpha t)$$

(3M)

Where, α be the temperature coefficient of resistance at 0°C

$$\alpha = \frac{R_t - R_0}{R_0 t}$$

$$R_0 = \frac{R_t}{1 + \alpha t}$$


Note: The resistivity like resistance also increase with temperature and increase is given by

$$\rho_t = \rho_0 (1 + \alpha t)$$

of a conductor

Direct and Alternating Current:

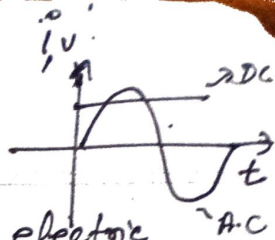In alternating current (AC), the flow of electronic charge periodically reverses direction, whereas in direct current (DC) the flow of electronic charge is only in one direction.



(9) (C)

* Difference between DC and AC.

<u>D.C</u>	<u>A.C</u>
1) The value of D.C. is steady constant at any time.	1) The value of A.C. changes continuously.
2) The value of D.C. is generated by chemical reaction is. Batteries, solar energy	2) A.C. is generated by the relative motion of magnetic field & the conductor.
3) Effect of D.C. on resistance, capacitance & inductance is not different	3) Effect of AC in all these elements are different.
4) DC current flow in only one direction.	4) A.C. current first flows in one direction & then in opposite direction.

#

Electrical power and Energy

Electric power : It is the rate of doing work

$$\text{i.e. } P = \frac{W}{t} = \frac{\text{Joules}}{\text{Sec}} = \text{Watt}$$

where,

P = power in watts

W = Work done in joule

t = time in second.

$$\boxed{1 \text{ kWh} = 1000 \text{ Watt}}$$

$$1 \text{ unit} = 1 \text{ kWh}$$

$$= 1000 \times 60 \times 60 \dots$$

* Power in Electric Circuit:

$$P = VI$$

$$\therefore V = IR \quad [\text{According to Ohm's law}]$$

$$\therefore P = IR \cdot I$$

$$\text{or, } P = I^2 R$$

$$\text{or, } P = VI = V \cdot \frac{V}{R} = \frac{V^2}{R}$$

$$\therefore \boxed{P = VI = I^2 R = \frac{V^2}{R}}$$

The power is also measured in h.p

$$\therefore 1 \text{ hp} = 746 \text{ Watt}$$

* Electrical Energy:

Energy is the capacity of doing work. Energy may exist in several forms & may be changed from one form to another form.

For example: A generator changes mechanical energy into electrical energy & electrical radiator converts electrical energy to heat energy.

The m.k.s unit of energy is joule.

It is the workdone when the point of application of force of one newton is moved 1m in the direction of force.

$$\text{i.e. } W = F \times S$$

$$\text{or } J = 1 \text{ N} \times 1 \text{ m}$$

$$\therefore 1 J = 0.7375$$

Numerical Q. (1)

A coil consists of 2,000 turns of copper wire having a cross-sectional area of 0.8 mm^2 . The mean length per turn is 80 cm and the resistivity of copper is $0.02 \mu\Omega/\text{m}$. Find the resistance of the coil.

Solution: and power absorbed by the coil when connected across 110 V d.c supply

Length of the coil, $l = 0.8 \times 2000$ [$\because 80 \text{ cm} = 0.8 \text{ m}$]
 $= 1600 \text{ m}$

$$A = 0.8 \text{ mm}^2 = 0.8 \times 10^{-6} \text{ m}^2$$

We know, $R = \rho \frac{l}{A} = 0.02 \times \frac{1600}{0.8 \times 10^{-6}}$
 $= 0.02 \times 10^{-6} \times \frac{1600}{0.8 \times 10^{-6}}$

$$= 40 \Omega$$

given,

$$\rho = 0.02 \mu\Omega/\text{m}$$

$$A = 0.8 \text{ mm}^2$$

Also on

$$\rho = 0.02 \Omega/\text{m}$$

$$\text{Ans } R = 40000000 = 4 \times 10^4 \text{ k}\Omega$$

$$\text{Power absorbed} = \frac{V^2}{R} = \frac{110^2}{40}$$

$$= 302.5 \text{ W}$$

②. A conductor of copper at 20°C is ~~is~~ with its resistance 8Ω is heated to 25°C . find the resistance of conductor at 25°C . Temp. coefficient of copper at 20°C is 39.3×10^{-4} .

$\Rightarrow$

given, Resistance at 20°C , $R_{20} = 8 \Omega$, $\alpha = 39.3 \times 10^{-4}$

$$R_{25} = ?$$

$$R_t = R_0(1 + \alpha t)$$

rise in temp, $(t = 25^\circ\text{C} - 20^\circ\text{C})$
 $= 5^\circ\text{C}$

$$\rho_{\text{Aluminium at } 20^{\circ}\text{C}} = 28 \times 10^{-8} \frac{\Omega \cdot \text{m}}{\text{m}} \times 1.0393 = 0.02842 \frac{\Omega \cdot \text{m}}{\text{m}} \times 1.0393$$

$$\therefore R_{25} = R_{20}(1 + \alpha t)$$

$$\begin{aligned} \text{or, } R_{25} &= 8(1 + 39.3 \times 10^{-4} \times 5) \\ &= 8(1 + 5 \times 39.3 \times 10^{-4}) \\ &= 8.1572 \Omega \end{aligned}$$

③. Length of the Copper Conductor is 300 m, with cross-sectional area (A) 0.6 mm^2 . Find the resistance of Conductor if the resistivity of Copper wire is $0.017 \mu\Omega\text{-m}$.

⇒ given,

$$\text{Length (l)} = 300 \text{ m}$$

$$\text{C-area (A)} = 0.6 \text{ mm}^2 = 0.6 \times 10^{-6} \text{ m}^2$$

$$\begin{aligned} \rho &= 0.017 \mu\Omega\text{-m} = 0.017 \times \frac{1}{10^6} \Omega\text{-m} \\ &= 0.017 \times 10^{-6} \Omega\text{-m} \\ &= 1.7 \times 10^{-8} \Omega\text{-m} \end{aligned}$$

$$R = ?$$

$$\therefore R = \rho \frac{l}{A}$$

$$= 1.7 \times 10^{-8} \times \frac{300}{0.6 \times 10^{-6}}$$

$$= 1.7 \times 10^{-2} \times \frac{300}{0.6}$$

$$= \frac{1.7 \times 300}{100 \times 0.6}$$

$$= 8.5 \Omega$$

Answer

$$\begin{aligned} A &= 0.6 \text{ mm}^2 \\ &= 0.6 \times \frac{1}{1000} \times \frac{1}{1000} \text{ m}^2 \\ &= 0.6 \times 10^{-6} \text{ m}^2 \end{aligned}$$

Unit: 2 Electric Circuit fundamentals

2.1) Electric Current and Voltage

2.2) Circuit elements: Resistor, Capacitor, Inductor

* Resistor: A resistor is a passive two terminal component that implements electrical resistance as a circuit element.

The current through the resistor is directly proportional to the voltage across the resistor's terminal. This relation is represented by ohm's law:


$$I = \frac{V}{R}$$

Where,

I = ekt. current in Ampere

V = A.d measured across the
conductor in Volt

R = Resistance of the conductor in ohm.

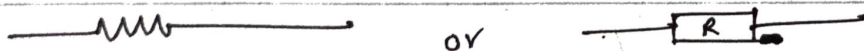

Symbol of resistor.

* Inductor:

An inductor is also called a coil or, reactor is a passive two terminal electrical component which resists changes in electric current.

passing through it.



Symbol of Inductor / coil.

It consists of a Conductor such as wire, usually wound into a coil. When a current flows through it, energy is stored in a magnetic field in the coil. When the current flowing through the inductor changes, the time varying magnetic field induces a voltage in the conductor according to Faraday's law of electromagnetic induction.

* Capacitor:

A capacitor is also known as Condenser. Condenser / Capacitor is a passive two terminal component used to store energy electrostatically in an electric field. There are various forms of capacitor but all contain at least two electrical conductors separated by a dielectric.



Symbol of Capacitor.

2.3) Voltage and Current Source

Voltage Source: Any device that produces voltage output (o/p) continuously is known as a Voltage Source. Example: Cells and d.c generators

Current Source : Any device that produce current o/p continuously is known as Current Sources.

Resistance in Series:

When some conductor having resistances R_1, R_2, R_3 etc are joined end to end as shown in fig: (1) they are said to be connected in series


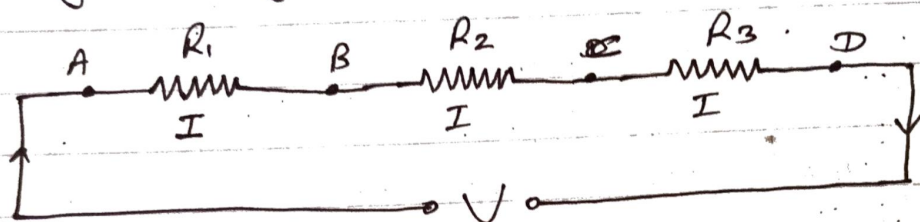


Fig: 1

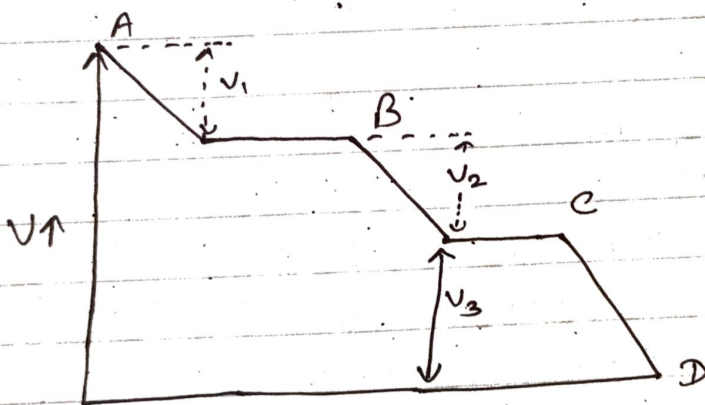

It can be proved that the equivalent resistance or, total resistance (R_T or R_{eq}) between points A and D is equal to the sum of the three individual resistance.

In Series Connection of resistance, it should be noted that:

1) Current is same through all the resistance

$$\text{i.e. } I = I_1 = I_2 = I_3 = I_n$$

2) Voltage drop across each resistance is different
or, voltage is different in all resistance.

$$\text{i.e. drop in } R_1 = V_1$$

$$\text{" " } R_2 = V_2$$

$$R_3 = V_3$$

3) Sum of the voltage drop is equal to the applied voltage across the resistances.

$$\text{i.e. } V = V_1 + V_2 + V_3$$

Applying Ohm's law

$$V = IR$$

$$\text{or, } IR = I_1 R_1 + I_2 R_2 + I_3 R_3 \quad [\because V = V_1 + V_2 + V_3]$$

$$\text{or, } IR = I R_1 + I R_2 + I R_3$$

$$[\because I_1 = I_2 = I_3 = I]$$

$$\text{or, } IR = I (R_1 + R_2 + R_3)$$

$$\therefore \boxed{R = R_1 + R_2 + R_3}$$

$$\text{or, } \boxed{\Sigma R = R_1 + R_2 + R_3}$$

Where, R = equivalent or, total resistance
or ckt.


⊗ The main characteristics of a Series ckt. are:

- 1) Same current flow through all parts of the ckt.
- 2) Different resistor have their individual voltage drops.
- 3) Voltage drops are additive (added)
- 4) Applied voltage is equal to the sum of different voltage drops.
- 5) Resistance are additive (added)
- 6) Power are additive (added)

$$P_{\text{total}} = P_1 + P_2 + P_3$$

$$\text{or } VI = V_1 I_1 + V_2 I_2 + V_3 I_3$$
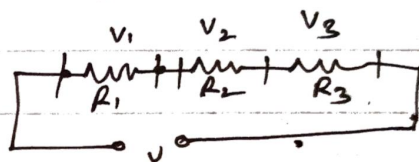
$$\text{or } VI = V_1 I + V_2 I + V_3 I$$




$$P_1 = V_1 I_1$$

$$P_2 = V_2 I_2$$

$$P_3 = V_3 I_3$$

* Voltage Divider Rule
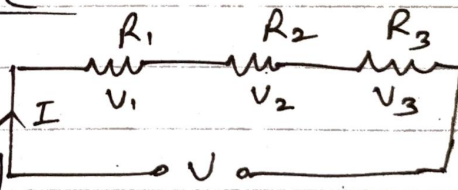
$$\text{Voltage drop} = \frac{\text{total Voltage} \times \text{Same resistor}}{\text{total resistance}(\Sigma R)}$$



$$\text{i.e. } V_1 = \frac{V \times R_1}{R_1 + R_2 + R_3} = \frac{V \times R_1}{\Sigma R}$$


$$V_2 = \frac{V \times R_2}{\Sigma R}$$

$$V_3 = \frac{V \times R_3}{\Sigma R}$$

$$\begin{aligned} \Sigma R &= R_1 + R_2 + R_3 \\ &= \text{Equivalent} \end{aligned}$$

Resistance in Parallel

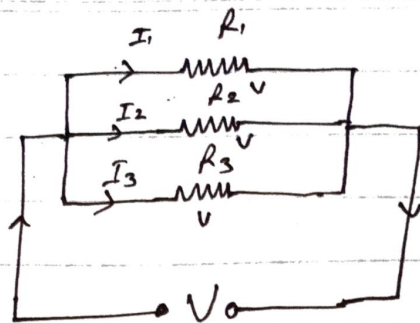Three resistances are joined as shown in fig:1. are said to be connected in parallel.



In this case,

1) P.d (V) across all resistor is same.

fig: 1

2) Current in each resistor is different & is given by ohm's law.

3) Total current is the sum of the three separate currents.

$$\therefore I = I_1 + I_2 + I_3$$

But, by ohm's law $V = IR$ or $I = \frac{V}{R}$

Where,

V = total or, applied voltage

R = equivalent resistance in the parallel combination

$$\therefore \frac{V}{R} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \quad [\because I = I_1 + I_2 + I_3]$$

$$\text{or, } \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \quad [\because V = V_1 = V_2 = V_3]$$

$$\text{or, } \frac{V}{R} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\text{or, } \boxed{\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

OR

$$\frac{1}{R} = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3}$$

$$\therefore \boxed{R = \frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2}}$$

* The main characteristics of Parallel ckt is:

1. The same voltage acts across all parts of resistances.
2. Different resistance have their individual (own) current
3. Branch currents are additive (added)
 $(I = I_1 + I_2 + I_3)$
4. Powers are additive
5. Conductance are additive.

* Conductance:

The reciprocal of resistance (R) is called Conductance (G).

$$\therefore G = \frac{1}{R} \quad 'R' \text{ ohm}$$

Unit of ' G ' = 'Mho' or 'Siemens'

In Series

$$R = R_1 + R_2$$

$$\text{or, } \frac{1}{G} = \frac{1}{G_1} + \frac{1}{G_2}$$

$$\therefore G = \frac{1}{R}$$

$$\therefore R = \frac{1}{G}$$

In Parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\text{or, } G = G_1 + G_2$$

Resistance in parallel

$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

* Current divider rule:


$$\therefore \boxed{V = IR}$$

Here, $I = I, R_1$

$$\therefore IR = I, R_1$$

$$\left[I_1 = \frac{IR}{R_1} = \frac{I}{R_1} \frac{R_1 R_2}{R_1 + R_2} = \frac{I R_2}{R_1 + R_2} \right]$$

$$R = R_1 \parallel R_2$$

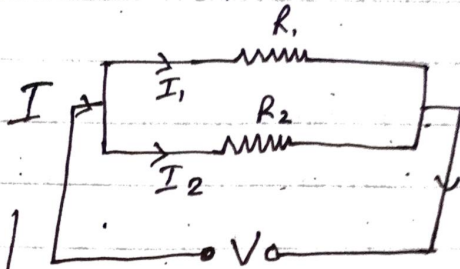

$\therefore$ Current divide = $\frac{\text{Total current} \times \text{Opposite resistance}}{\Sigma R}$


$$\therefore I_1 = \frac{I \times R_2}{R_1 + R_2}$$

$$I_2 = \frac{I \times R_1}{R_1 + R_2}$$

$$I_1 = I \left(\frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right)$$

$$I_2 = I \frac{R_1 R_3}{(R_1 R_2 + R_2 R_3 + R_3 R_1)}$$

$$I_3 = \frac{I (R_1 R_2)}{(\quad)}$$

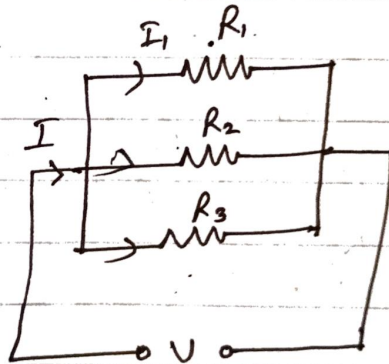

V.V.I.

Ohm's Law:

It states that, "the ratio of potential difference (V) between any two points of a ckt. or Conductor to the Current (I) flowing between them is constant, provided the temperature remains constant."

i.e.

$$\frac{V}{I} = \text{Constant.}$$

$$\text{or } \frac{V}{I} = R$$



Where, V = Voltage between two points

I = Current flowing in the conductor.

R = Resistance of the conductor.

$$\therefore \boxed{V = IR}$$

V.V.I.

Kirchhoff's point law or, Current law (KCL):

It states that, "In any electrical network, the algebraic sum of the current meeting at a point (or, Junction) is zero"

It means simply that total leaving current from a junction is equal to the total entering current to the junction.

Σ i.e. incoming current = outgoing current

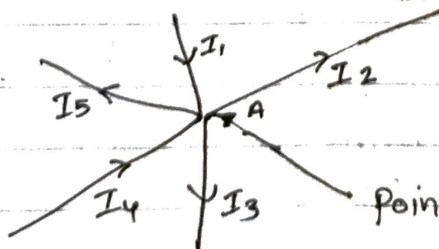


Fig: 9

Consider a few conductors meeting at a point 'A' as shown in fig: a. Some conductors have currents incoming, while some currents are outgoing.

Assuming the incoming currents to be +ve and the outgoing currents to be -ve, we have

$$I_1 + (-I_2) + (-I_3) + I_4 + (-I_5) = 0 \text{ or } \sum I = 0$$

$$\text{or, } I_1 - I_2 - I_3 + I_4 - I_5 = 0$$

$$\text{or, } I_1 + I_4 = I_2 + I_3 + I_5$$

$\therefore$ Incoming currents = outgoing currents.

Kirchoff's Mesh or Voltage Law (KVL):

It states that, "the algebraic sum of products of current & resistance in each of the conductor in any closed path or (mesh) in a network plus the algebraic sum of the emf's in that path is zero."

In other words:

$$\sum IR + \sum \text{e.m.f} = 0$$

(5N)

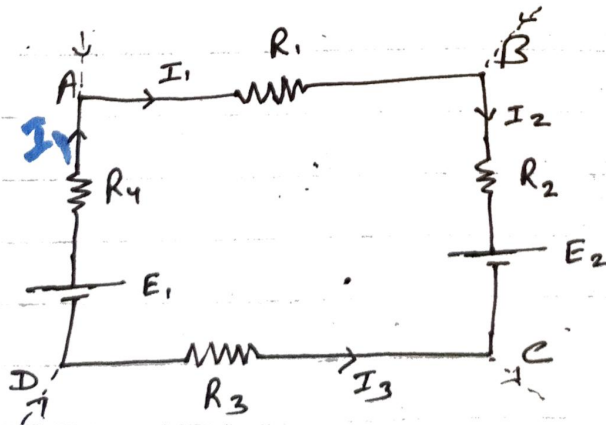


Fig: B


Consider the closed path ABCDA as shown in fig. b

using KVL, we get


$$-I_1 R_1 - I_2 R_2 + I_3 R_3 - I_4 R_4 - E_2 + E_1 = 0$$

$$\text{or, } I_1 R_1 + I_2 R_2 - I_3 R_3 + I_4 R_4 = E_1 - E_2 \quad //$$

a) Sign of Battery, e.m.f (EMF)

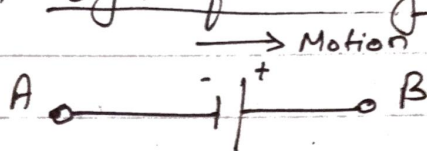


Rise in Voltage (+E)

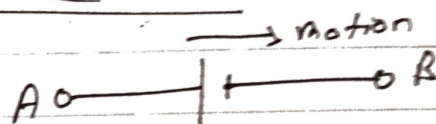


Fall in Voltage (-E)

b) Sign of IR drop

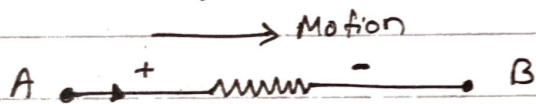

Fall in Voltage

$$V = (-IR)$$

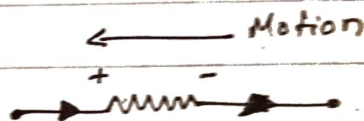


Rise in Voltage


$$V = (+IR)$$

Independent Source

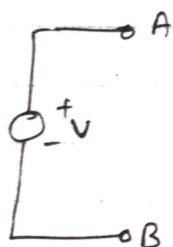
Those voltage or current sources, which do not depend on any other quantity in the ckt. are called independent source.




Independent
D.C Voltage
Source

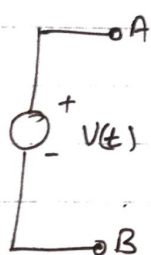

Time Varying
Independent
Voltage Source

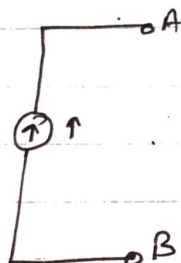


Independent
Current
Source

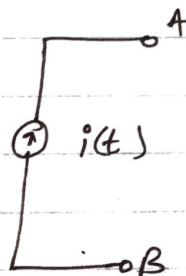


Time Varying
Current Source.

Dependent Source:

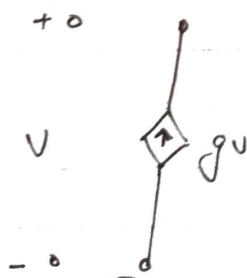A dependent voltage source or current source is one which depends on some quantity (current/voltage) in the circuit, which may be either voltage or current. Such a source is represented by a diamond shaped symbol as shown in figure below:



① Voltage dependent
Current Source

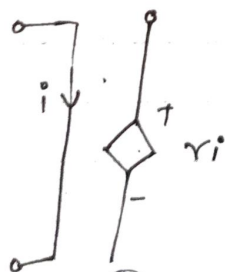

② Current dependent
Voltage Source

Numerical: chapter 1

1) If 10 metres of manganin-wire, 0.13 cm in diameter has a resistance of 3.4 ohms, Find the specific resistance of the material.

Solⁿ: diameter of wire (d) = 0.13 cm

Length of wire, l = 10 metre = 1000 cm

area of wire, $a = \frac{\pi d^2}{4} = \frac{\pi (0.13)^2}{4} = 0.01327 \text{ cm}^2$

$$1.327 \times 10^{-6} \text{ m}^2$$

Resistance of wire, $R = 3.4 \Omega$

Resistivity of wire, $\rho = ?$

We know, $R = \rho \frac{l}{a}$

$$\text{or, } \rho = \frac{Ra}{l} = \frac{3.4 \times 0.01327}{1000}$$

$$= 4.51 \times 10^{-5} \Omega \text{ cm}$$

$$4.51 \times 10^{-7} \Omega \text{ m}$$

Tutorial:

2) Calculate the resistance of 915 metres length of wire having a uniform cross-sectional area of 0.77 cm^2 if the wire is made of Copper having a resistivity of $1.7 \times 10^{-6} \Omega \text{ cm}$.

Solⁿ:

length (l) = 915 m = $915 \times 100 \text{ cm}$

area of cross-section (a) = 0.77 cm^2

resistivity of wire (ρ) = $1.7 \times 10^{-6} \Omega \text{ cm}$

$R = ?$

$$R = \rho \frac{l}{a} = 1.7 \times 10^{-6} \times \frac{91500}{0.77} = 0.2020 \Omega$$

note:

If a conductor has a resistance R_0 , R_t and R_2 at 0°C , $t_1^\circ\text{C}$ and $t_2^\circ\text{C}$ respectively, then

$$R_1 = R_0 (1 + \alpha_0 t_1) \quad \& \quad R_2 = R_0 (1 + \alpha_0 t_2)$$

$$\frac{R_2}{R_1} = \frac{1 + \alpha_0 t_2}{1 + \alpha_0 t_1}$$

$$\left[\begin{aligned} \alpha_0 &= \frac{R_t - R_0}{R_0 t} \\ R_0 &= \frac{R_t}{1 + \alpha_0 t} \\ R_t &= R_0 (1 + \alpha_0 t) \end{aligned} \right]$$

(2067) (new course)

- ③. The shunt winding of a motor has a resistance of 35.1Ω at 20°C . Find the resistance at 32.6°C . The temperature coefficient of copper is 0.00427°C at 0°C

Soln.

Given,

$$\alpha_0 = 0.00427/^\circ\text{C}$$

$$\text{Resistance at } 20^\circ\text{C}, R_{20} = 35.1 \Omega$$

finding resistance at 0°C ,

$$R_0 = \frac{R_t}{1 + \alpha_0 t}$$

$$\left[\alpha = \frac{R_t - R_0}{R_0 t} \right]$$

$$\therefore R_0 = \frac{R_{20}}{1 + \alpha \cdot 20}$$

$$= \frac{35.1}{1 + 0.00427 \times 20}$$

$$= \frac{35.1}{1 + 0.0854} = 32.33 \Omega$$

Now,

$$R_{32.6^\circ\text{C}} = R_0 (1 + \alpha_0 \times t)$$

$$= R_0 t \quad 32.33 (1 + 0.00427 \times 32.6) \\ = 36.83 \Omega$$

✓

④ The resistance of a Copper coil at 30°C is 0.18Ω
What is the resistance at 91.6°C ? For Copper, $\alpha_0 = 0.00427$

$\Rightarrow$

Given,

$$\alpha_0 = 0.00427/^\circ\text{C at } 0^\circ\text{C}$$

$$R_{30} = 0.18\Omega$$

$$R_{91.6} = ?$$

Now, finding resistance at 0°C

$$\begin{aligned} R_0 &= \frac{R_t}{1 + \alpha_0 t} = \frac{R_{30}}{1 + \alpha_0 \cdot 30} = \frac{0.18\Omega}{1 + 0.00427 \times 30} \\ &= \frac{0.18}{1.1281} \\ &= 0.159\Omega \end{aligned}$$

Therefore, $\therefore R_t = R_0 (1 + \alpha_0 t)$

$$\begin{aligned} R_{91.6} &= 0.159 (1 + 0.00427 \times 91.6) \\ &= 0.222\Omega \end{aligned}$$

Answer

directly
 0.227Ω
 0.22Ω

Chapter-2 (Numerical)

$$R = R_1 + R_2 \quad V_1 = \frac{V \times R_1}{R_{tot.}}$$


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad I_1 = \frac{I \times R_2}{R_{tot.}}$$

$$R = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad V = IR$$



A battery having an emf of 12V is connected across terminal AB of the circuit.

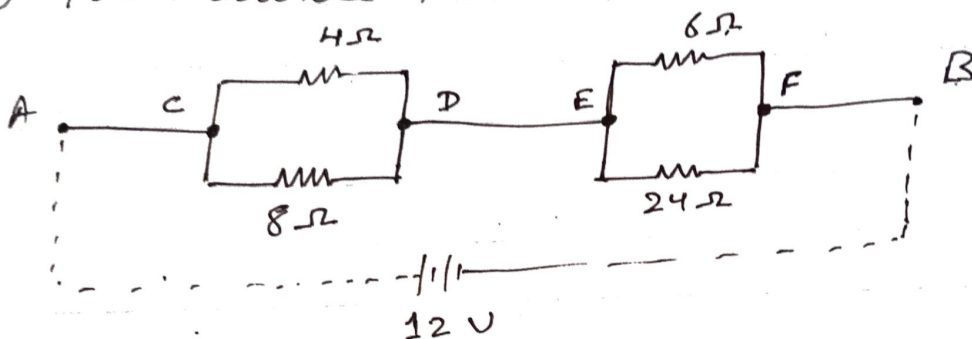- F (i) Current flowing in each resistance and
 (ii) total power absorbed by the ckt.
 (iii) Power absorbed in 24Ω resistor.



Solⁿ:

Resistance between C and D is calculated

$$\text{as } \frac{1}{R_{CD}} = \frac{1}{4} + \frac{1}{8} = \frac{3}{8} \Omega \text{ or } 0.375 \Omega$$

$$\therefore R_{CD} = \frac{8}{3} = 2.67 \Omega$$

$$\text{And } R_{EF} = \frac{24 \times 6}{24 + 6} = \frac{144}{30} = 4.8 \Omega$$

$\therefore$ Resistance between A and B is $R_{CD} + R_{EF}$

$$R_{AB} = R_{CD} + R_{EF}$$

$$= 2.67 + 4.8 = 7.47 \Omega$$

$$\text{Total circuit current, } I = \frac{V}{R_{AB}} = \frac{12}{7.47} = 1.606 \text{ A}$$

$$\begin{aligned} \text{Voltage between C \& D, } V_{CD} &= I \times R_{CD} \\ \therefore V_{CD} &= 1.606 \times 2.67 \\ &= \underline{4.289 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{Voltage between E \& F, } V_{EF} &= I \times R_{EF} \\ \therefore V_{EF} &= 1.606 \times 4.8 \\ &= \underline{7.708 \text{ V}} \end{aligned}$$

(i) Current through 4Ω resistor,

$$\therefore V = IR, \quad I = \frac{V_{CD}}{R} \quad \boxed{V = V_{CD} = 4.289 \text{ V}}$$

$$I_{4\Omega} = \frac{4.289}{4} = 1.072 \text{ A}$$

$$I_{8\Omega} = \frac{4.289}{8} = 0.5361 \text{ A}$$

$$I_{6\Omega} = \frac{V_{EF}}{6} = \frac{7.708}{6} = 1.284 \text{ A}$$

$$I_{24\Omega} = \frac{V_{EF}}{24} = \frac{7.708}{24} = 0.3211 \text{ A}$$

(ii) Power absorbed by circuit (P) $I^2 R = (1.606)^2 \times 7.47$
 $= 19.27 \text{ Watts}$

$$\begin{aligned} \text{or, } P &= VI \\ &= 12 \times 1.606 \end{aligned}$$


$$= \underline{19.27 \text{ Watts.}}$$

(iii) Power absorbed by 24Ω resistor,

$$P_{24\Omega} = (0.3211)^2 \times 24 = \underline{2.47 \text{ Watts}}$$

$$\begin{aligned} \text{or, } P_{24\Omega} &= V_{EF} \times I_{24\Omega} = 7.708 \times 0.3211 \\ &= \underline{2.47 \text{ Watts}} \end{aligned}$$

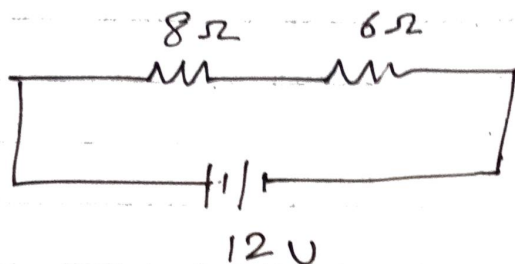- ② Find (i) Circuit current and (ii) Voltage drop on resistors 8Ω and 6Ω , across $12V$ emf.



Solⁿ:

$$R_{\text{equivalent}} = 8 + 6 = 14\Omega$$

$$V = 12V$$

(i) Total current through circuit I

$$I = \frac{V}{R_{\text{eq}}} = \frac{12}{14} = 0.857A$$

(ii) Voltage across 8Ω resistor.

$$\begin{aligned} V_8 &= I \times 8 \\ &= 0.857 \times 8 \\ &= 6.856V \end{aligned}$$

$$\begin{aligned} \text{or, } V_8 &= \frac{V \times 8}{R_{\text{eq}}} \\ &= \frac{12 \times 8}{14} \\ &= 6.85V \end{aligned}$$

Voltage across 6Ω resistor

$$\begin{aligned} V_6 &= I \times 6 \\ &= 0.857 \times 6 \\ &= 5.142V \end{aligned}$$

$$\begin{aligned} \text{or, } V_6 &= \frac{V \times 6}{R_{\text{eq}}} \\ &= \frac{12 \times 6}{14} \\ &= 5.14V \end{aligned}$$

(iii) Power absorbed

$$\begin{aligned} P &= VI = 12 \times 0.857 \\ &= 10.28 \text{ Watts} \end{aligned}$$

$$\text{or } I^2 R = 10.28 \text{ Watts}$$


- ③. Three resistors 4Ω , 12Ω , 6Ω are connected in parallel. If the total current taken is $12A$, find the current through each resistor.

Soln:

Total equivalent
Resistance.

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{12} + \frac{1}{6} = \frac{6}{12}$$

$$R_T = \frac{12}{6} = 2\Omega$$

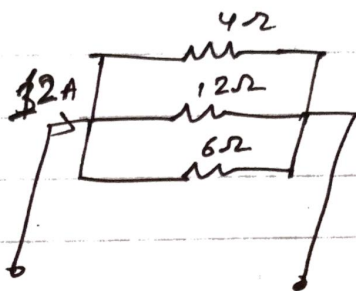

(P.) Voltage across the circuit $= I R_T$
 $= 12 \times 2$
 $= 24V$


Current through $4\Omega = \frac{24}{4}$ $\left[\because I = \frac{V}{R} \right]$
 $= 6A$

" " $12\Omega = \frac{24}{12} = 2A$

$6\Omega = \frac{24}{6} = 4A$

2068

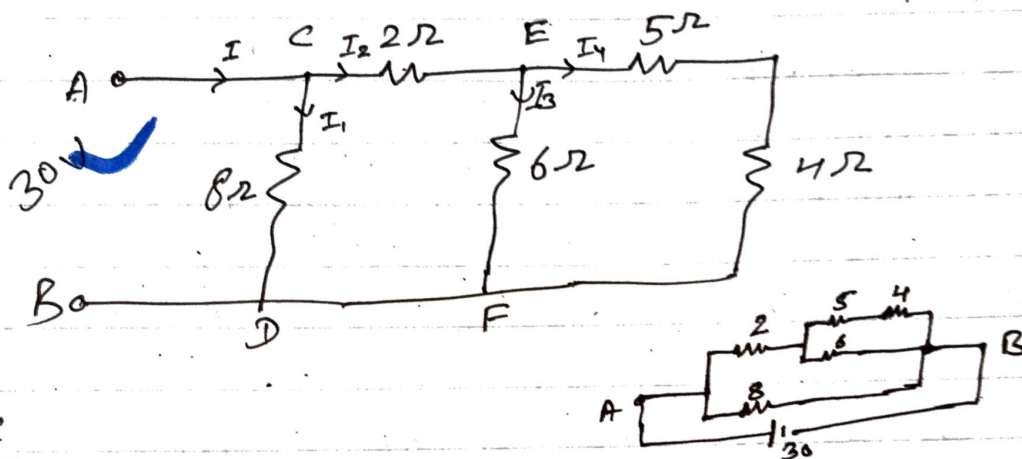- 4) A battery of 30 V is applied across terminal AB of the circuit in figure. The current in 5Ω resistor will be what?



Solⁿ:

Resistance between E and F,

$$R_{EF} = \frac{(5+4) \times 6}{(5+4) + 6} = \frac{54}{15} = 3.6 \Omega$$

Total Resistance between C and D, i.e. betⁿ A & B

$$\text{Total Resist } R_{AB} = R_{CD} = \frac{(2 + 3.6) \times 8}{(2 + 3.6) + 8} = \frac{44.8}{13.6} = 3.29 \Omega$$

Now,

(i) Total Circuit Current (I) = $\frac{V}{R_{AB}} = \frac{30}{3.29}$
 Current from battery,
 $= 9.107 \text{ A}$

(ii) Current through 8Ω resistor,

$$I_1 = \frac{V}{R} = \frac{30}{8} = 3.75 \text{ A}$$

(iii) Current through 2Ω resistor,

$$I_2 = I - I_1 = 9.107 - 3.75 = 5.357 \text{ A}$$

potent P.D across EF = $30 - (5.357 \times 2)$

$$V_{EF} = 19.286 \text{ V}$$

(iv) Current through 6Ω resistor = $\frac{V_{EF}}{R}$

$$= \frac{19.286}{6}$$



$$I_3 = 3.214 \text{ A}$$

(v) $\therefore$ current through 5Ω resistor is

$$\begin{aligned} I_4 &= I_2 - I_3 & (\because I_2 = I_4 + I_3) \\ &= 5.357 - 3.214 \\ &= 2.142 \text{ A} \end{aligned}$$

Equivalent resistance

Star to Delta.

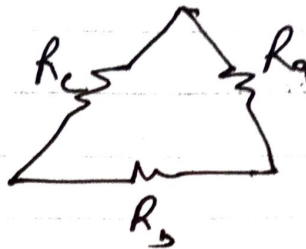
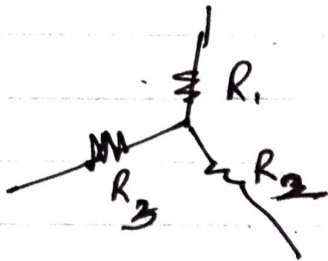


$$R_a = \frac{R_1 \cdot R_2 + R_1 \cdot R_3 + R_2 \cdot R_3}{R_3}$$

$$R_b = \frac{R_1 \cdot R_2 + R_1 \cdot R_3 + R_2 \cdot R_3}{R_1}$$

$$R_c = \frac{\text{"}}{R_2}$$

Delta to Star

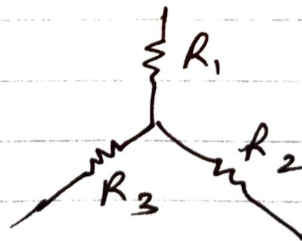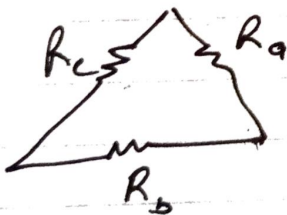

$$R_1 = \frac{R_a \cdot R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}$$